

```
not gate:
module not_gate(output out,input in);
not(out,in);
endmodule
```

```
module not_gate_tb;
reg in;
wire out;
not_gate obj (out,in);
initial begin
in=0;
#1 in=1;
end
```

```
initial begin
$monitor("T=%t in=%b out=%b",$time,in,out);
end
endmodule
```

```
-----
and gate:
module and_gate(output out,input in1,input in2);
and(out,in1,in2);
endmodule
```

```
module and_gate_tb;
reg in1,in2;
wire out;
and_gate obj (out,in1,in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end
```

```
initial begin
$monitor("T=%t in1=%b in2=%b out=%b",$time,in1,in2,out);
end
endmodule
```

```
-----
or gate:
module or_gate(output out,input in1,input in2);
or(out,in1,in2);
endmodule
```

```
module or_gate_tb;
reg in1,in2;
wire out;
or_gate obj (out,in1,in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end
```

```
initial begin
$monitor("T=%t in1=%b in2=%b out=%b", $time, in1, in2, out);
end
endmodule
```

```
-----
nand gate:
module nand_gate(output out, input in1, input in2);
nand(out, in1, in2);
endmodule
```

```
module nand_gate_tb;
reg in1, in2;
wire out;
nand_gate obj (out, in1, in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end
```

```
initial begin
$monitor("T=%t in1=%b in2=%b out=%b", $time, in1, in2, out);
end
endmodule
```

```
-----
nor gate:
module nor_gate(output out, input in1, input in2);
nor(out, in1, in2);
endmodule
```

```
module nor_gate_tb;
reg in1, in2;
wire out;
nor_gate obj (out, in1, in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end
```

```
initial begin
$monitor("T=%t in1=%b in2=%b out=%b", $time, in1, in2, out);
end
endmodule
```

```
-----
module xor_gate(output out, input in1, input in2);
xor(out, in1, in2);
endmodule
```

```
module xor_gate_tb;
reg in1, in2;
wire out;
```

```

xor_gate obj (out,in1,in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end

```

```

initial begin
$monitor("T=%t in1=%b in2=%b out=%b", $time,in1,in2,out);
end
endmodule

```

```

-----
xnor:
module xnor_gate(output out,input in1,input in2);
xnor(out,in1,in2);
endmodule

```

```

module xnor_gate_tb;
reg in1,in2;
wire out;
xnor_gate obj (out,in1,in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end

```

```

initial begin
$monitor("T=%t in1=%b in2=%b out=%b", $time,in1,in2,out);
end
endmodule

```

```

-----
half adder:
module half_add(output sum1,output carry,input in1,input in2);
assign sum1=in1^in2;
assign carry=in1&in2;
endmodule

```

```

module half_add_tb;
reg in1,in2;
wire sum1,carry;
half_add obj (sum1,carry,in1,in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end

```

```

initial begin
$monitor("T=%t in1=%b in2=%b sum=%b carry=%b", $time,in1,in2,sum1,carry);
end
endmodule

```

full adder:

```
module full_add(output sum1,output carry_out,input in1,input in2,input carry_in);
assign sum1=carry_in^(in1^in2);
assign carry_out=in1&in2|carry_in&(in1^in2);
endmodule
```

```
module full_add_tb;
reg in1,in2,carry_in;
wire sum1,carry_out;
full_add obj (sum1,carry_out,in1,in2,carry_in);
initial begin
in1=0; in2=0; carry_in=0;
#1 in1=0; in2=0; carry_in=1;
#1 in1=0; in2=1; carry_in=0;
#1 in1=0; in2=1; carry_in=1;
#1 in1=1; in2=0; carry_in=0;
#1 in1=1; in2=0; carry_in=1;
#1 in1=1; in2=1; carry_in=0;
#1 in1=1; in2=1; carry_in=1;
end
```

```
initial begin
$monitor("T=%t in1=%b in2=%b carry_in=%b sum=%b carry=%b",$time,in1,in2,carry_in,sum1,carry_out);
end
endmodule
```

half sub:

```
module half_sub(output diff,output borrow,input in1,input in2);
assign diff=(~in1&in2)|(in1&~in2);
assign borrow=~in1&in2;
endmodule
```

```
module half_sub_tb;
reg in1,in2;
wire diff,borrow;
half_sub obj (diff,borrow,in1,in2);
initial begin
in1=0; in2=0;
#1 in1=0; in2=1;
#1 in1=1; in2=0;
#1 in1=1; in2=1;
end
```

```
initial begin
$monitor("T=%t in1=%b in2=%b diff=%b borrow=%b",$time,in1,in2,diff,borrow);
end
endmodule
```

full sub:

```
module full_sub(output diff,output borrow_out,input in1,input in2,input borrow_in);
assign diff=(in1^in2)^borrow_in;
assign borrow_out=(in1&~in2)&(in1&~borrow_in)&(in2&borrow_in);
endmodule
```

```

module full_sub_tb;
reg in1,in2,borrow_in;
wire diff,borrow_out;
full_sub obj (diff,borrow_out,in1,in2,borrow_in);
initial begin
in1=0; in2=0; borrow_in=0;
#1 in1=0; in2=0; borrow_in=1;
#1 in1=0; in2=1; borrow_in=0;
#1 in1=0; in2=1; borrow_in=1;
#1 in1=1; in2=0; borrow_in=0;
#1 in1=1; in2=0; borrow_in=1;
#1 in1=1; in2=1; borrow_in=0;
#1 in1=1; in2=1; borrow_in=1;
end

```

```

initial begin
$monitor("T=%t in1=%b in2=%b borrow_in=%b diff=%b borrow_out=%b", $time,in1,in2,borrow_in,diff,borrow_out);
end
endmodule

```

BCD-EXCESS 3

```

module BCD2Ex3(a,b,c,d,w,x,y,z);
    input a,b,c,d;
    output w,x,y,z;
    assign w= a |(b&c) | (b&d);
    assign x=(~b&c) | (~b&d) |(b&~c&~d);
    assign y= ~(c^d);
    assign z=~d;
endmodule

module test;
    reg a,b,c,d;
    wire w, x, y, z;
    BCD2Ex3 objt(a,b,c,d,w,x,y,z);
    initial
    begin
        $display("a\tb\tc\td\tw\tx\ty\tz");
        $monitor("%b\t%b\t%b\t%b\t%b\t%b\t%b\t%b",a,b,c,d,w,x,y,z);
        a=0; b=0; c=0; d=0;
        #10 a=0; b=0; c=0; d=1;
        #10 a=0; b=0; c=1; d=0;
        #10 a=0; b=0; c=1; d=1;
        #10 a=0; b=1; c=0; d=0;
        #10 a=0; b=1; c=0; d=1;
        #10 a=0; b=1; c=1; d=0;
        #10 a=0; b=1; c=1; d=1;
        #10 a=1; b=0; c=0; d=0;
        #10 a=1; b=0; c=0; d=1;
    end
endmodule

```

Excess3 to BCD

```

module Ex3toBCD(a,b,c,d,w,x,y,z);
    input a,b,c,d;
    output w,x,y,z;

```

```

    assign w= (a&b)|(a&c&d);
    assign x=(~b&~c)|(~b&~d)|(b&c&d);
    assign y= (~c&d)|(c&~d);
    assign z=~d;
endmodule
module test;
    reg a,b,c,d;
    wire w, x, y, z;
    Ex3toBCD obj(a,b,c,d,w,x,y,z);
    initial
    begin
        $display("a\tb\tc\td\tw\tx\ty\tz");
        $display("0\t0\t0\t0\tx\tx\tx\tx");
        $display("0\t0\t0\t1\tx\tx\tx\tx");
        $display("0\t0\t1\t0\tx\tx\tx\tx");
        $monitor("%b\t%b\t%b\t%b\t%b\t%b\t%b\t%b",a,b,c,d,w,x,y,z);

        a=0; b=0; c=1;d=1;
        #10 a=0; b=1; c=0;d=0;
        #10 a=0; b=1; c=0;d=1;
        #10 a=0; b=1; c=1;d=0;
        #10 a=0; b=1; c=1;d=1;
        #10 a=1; b=0; c=0;d=0;
        #10 a=1; b=0; c=0;d=1;
    end
endmodule

```

4x1 mux

```

module mux1( select, d, q );

```

```

    input[1:0] select;
    input[3:0] d;
    output    q;

```

```

    wire    q;
    wire[1:0] select;
    wire[3:0] d;

```

```

    assign q = d[select];

```

```

endmodule

```

```

module mux_tb;

```

```

    reg[3:0] d;
    reg[1:0] select;
    wire    q;

```

```

    integer i;

```

```

    mux1 my_mux( select, d, q );

```

```

    initial
    begin
        #1 $monitor("d = %b", d, " | select = ", select, " | q = ", q );
    end
endmodule

```

```

for( i = 0; i <= 15; i = i + 1)
begin
    d = i;
    select = 0; #1;
    select = 1; #1;
    select = 2; #1;
    select = 3; #1;
    $display("-----");
end

end
endmodule

-----

1x4 demux
module Demultiplexer_1_to_4_case (output reg [3:0] Y, input [1:0] A, input din);
always @(Y, A) begin
    case (A)
        2'b00 : begin Y[0] = din; Y[3:1] = 0; end
        2'b01 : begin Y[1] = din; Y[0] = 0; end
        2'b10 : begin Y[2] = din; Y[1:0] = 0; end
        2'b11 : begin Y[3] = din; Y[2:0] = 0; end
    endcase
end
endmodule

module Demultiplexer_1_to_4_case_tb;
wire [3:0] Y;
reg [1:0] A;
reg din;
Demultiplexer_1_to_4_case I0 (Y, A, din);
initial begin
    din = 1;
    A = 2'b00;
    #1 A = 2'b01;
    #1 A = 2'b10;
    #1 A = 2'b11;
end
initial begin
    $monitor("%t| Din = %d| A[1] = %d| A[0] = %d| Y[0] = %d| Y[1] = %d| Y[2] = %d| Y[3] = %d",
        $time, din, A[1], A[0], Y[0], Y[1], Y[2], Y[3]);
end
endmodule

-----

3x8 decoder
module decoder3_to_8( in,out, en);
input [2:0] in;
input en;
output [7:0] out;
reg [7:0] out;

always @( in or en)
begin

    if (en)

```

```

begin
    out=8'd0;
    case (in)
        3'b000: out[0]=1'b1;
        3'b001: out[1]=1'b1;
        3'b010: out[2]=1'b1;
        3'b011: out[3]=1'b1;
        3'b100: out[4]=1'b1;
        3'b101: out[5]=1'b1;
        3'b110: out[6]=1'b1;
        3'b111: out[7]=1'b1;
        default: out=8'd0;
    endcase
end
else
out=8'd0;
end
endmodule

module decoder_tb;
wire [7:0] out;
reg en;
reg [2:0] in;
integer i;

decoder3_to_8 dut(in,out,en);

initial begin
$monitor( "en=%b, in=%d, out=%b ", en, in, out);
for ( i=0; i<16; i=i+1)
begin
{en,in} = i;
#1;
end
end
endmodule

```

```

8x3 encoder
module encoder8x3(in,out);
input [7:0] in;
output [2:0] out;
reg [2:0] out;
reg [2:0] i;
always @(in)
begin
for(i=0;i<8;i=i+1)
if(in[i])
out=i;
end
endmodule

```

```

2x4 decoder
module Decoder(s1, s0, o0, o1, o2, o3);
input s1, s0;

```



```

output o0, o1, o2, o3;
wire s1_inv, s0_inv;

not(s1_inv, s1);
not(s0_inv, s0);
and(o0, s1_inv, s0_inv);
and(o1, s1_inv, s0);
and(o2, s1, s0_inv);
and(o3, s1, s0);
endmodule

```

```

module TestMod;

```

```

reg s1, s0;
wire o0, o1, o2, o3;

```

```

Decoder dec(s1, s0, o0, o1, o2, o3);

```

```

initial begin
$display("Time \t s1 \t s0 \t o0 \t o1 \t o2 \t o3");
$display("-----");
$monitor("%0d \t %b \t %b \t %b \t %b \t %b \t %b", $time, s1, s0, o0, o1, o2, o3);
end

```

```

initial #3 $finish;

```

```

initial begin
s1= 0; s0= 0;
#1;
s1= 0; s0= 1;
#1;
s1= 1; s0= 0;
#1;
s1= 1; s0= 1;
end
endmodule

```

```

-----
4x2 encoder
`timescale 1ns / 1ps
module encoder42(
    input D0,
    input D1,
    input D2,
    input D3,
    output Q0,
    output Q1,
    output V
);
wire a1, nD1;

```

```

not(nD1, D1);
and(a1, nD1, D2);

```

```

or(Q0, D0, D1);
or(Q1, a1, D0);

```

```
or(V, D0, D1, D2, D3);
```

```
endmodule
```

```
`timescale 1ns / 1ps
```

```
module encoder42_tb;
```

```
    // Inputs
```

```
    reg D0;
```

```
    reg D1;
```

```
    reg D2;
```

```
    reg D3;
```

```
    // Outputs
```

```
    wire Q0;
```

```
    wire Q1;
```

```
    wire V;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    encoder42 uut (
```

```
        .D0(D0),
```

```
        .D1(D1),
```

```
        .D2(D2),
```

```
        .D3(D3),
```

```
        .Q0(Q0),
```

```
        .Q1(Q1),
```

```
        .V(V)
```

```
    );
```

```
    initial begin
```

```
        // Initialize Inputs
```

```
        D0 = 1;
```

```
        D1 = 0;
```

```
        D2 = 0;
```

```
        D3 = 0;
```

```
        // Wait 100 ns for global reset to finish
```

```
        #100;
```

```
        D0 = 0;
```

```
        D1 = 1;
```

```
        D2 = 0;
```

```
        D3 = 0;
```

```
        #100;
```

```
        D0 = 0;
```

```
        D1 = 0;
```

```
        D2 = 1;
```

```
        D3 = 0;
```

```
        #100;
```

```
        D0 = 0;
```

```
        D1 = 0;
```

```
        D2 = 0;
```

```
        D3 = 1;
```

// Add stimulus here

end

endmodule
